




Construct truth tables for functions 1

A	B	F
0	0	1
1	0	0
0	1	0
1	1	1

A	B	G
0	0	1
1	0	0
0	1	0
1	1	0

1.1

 = 1  = 0

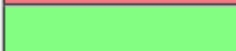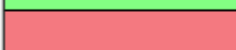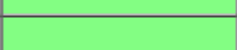button 1	button 2	alarm	door result
			
			
			
			
			
			
			
			

1.2

Expressions for functions F and G are given below.

Calculate the values of both functions when $A = 0$, $B = 1$ and $C = 1$.

$$F = \bar{A} \cdot C + B \cdot \bar{C}$$


$$G = (A + B) \cdot (\bar{B} + \bar{C})$$

Write your answer here!



$$F = (1 \text{ and } 1) \text{ or } (1 \text{ and } 0) = 1 = \text{True}$$

$$G = (0 \text{ or } 1) \text{ and } (0 \text{ or } 0) = 0 = \text{False}$$

1.3

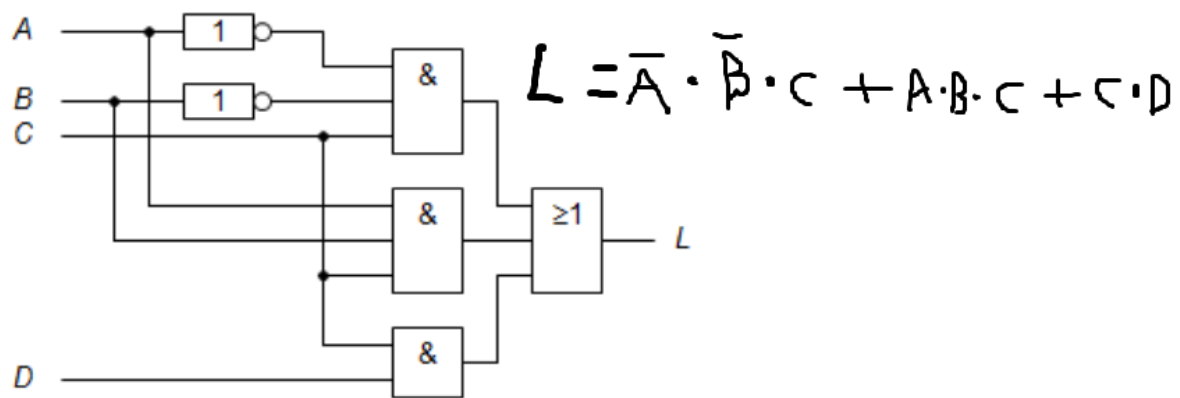


1.4

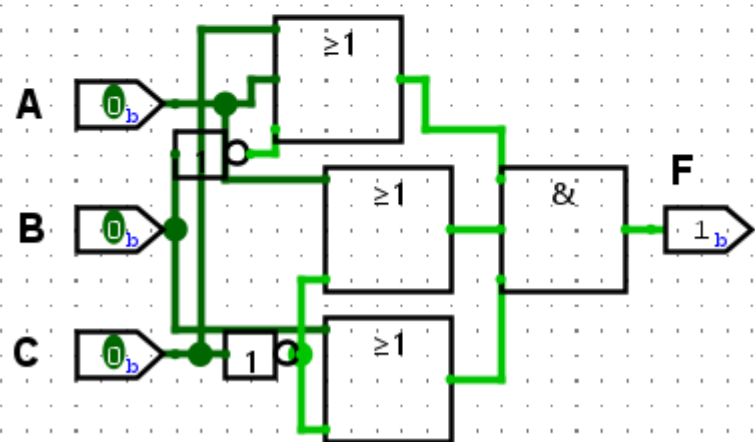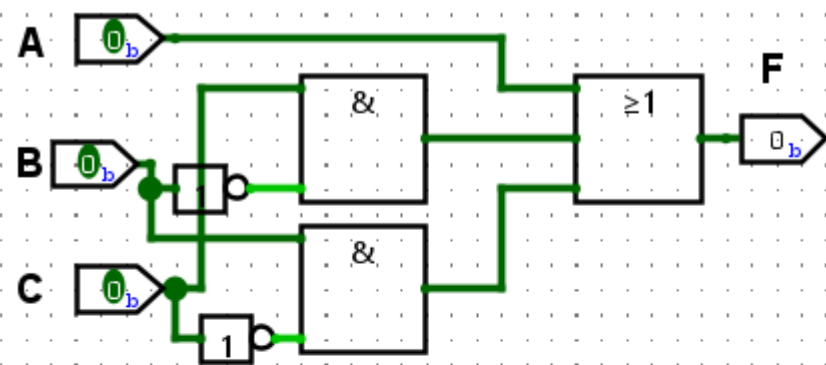

1.5

Inspection switch

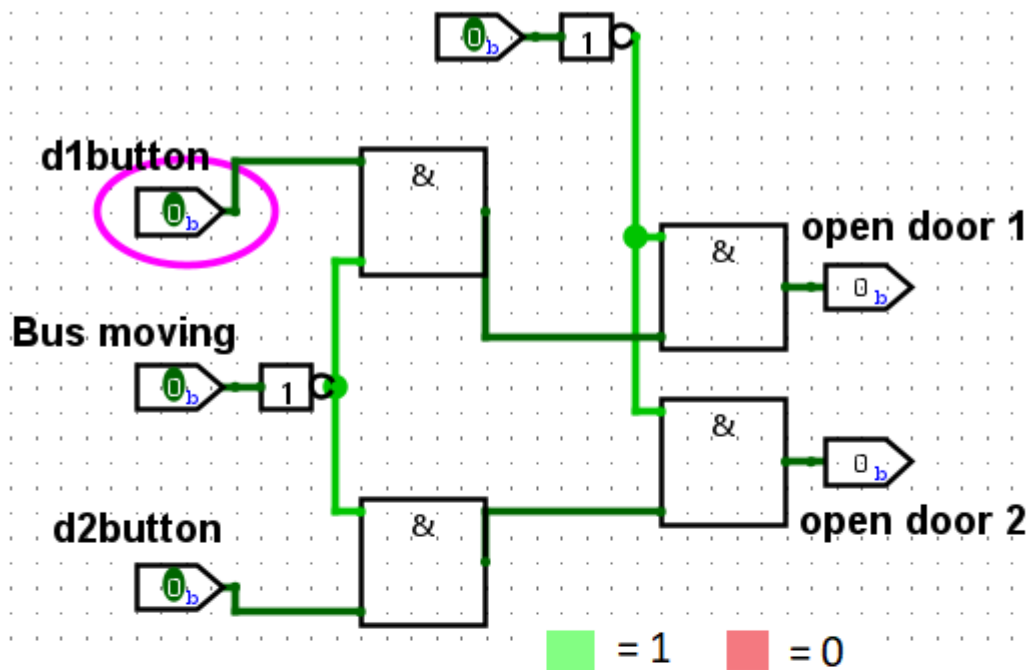[illegible]